

Light it up!

Join the dots. Then choose a conductor that could complete the circuit and light the bulb. A conductor is anything that lets electricity flow through it. Circle the two things that would work and write the letters in the boxes at the bottom of the page.

1
2
3
4
5
6

a b c
d e
f
g h i
j k
l

Conductors

--	--	--